

Lab Report number 5

Wheatstone Bridge

ENS203 – Electrical Circuits I

Emre Arapcic-Uevak
220302289

Afan Haznadarevic
220302128

Assistant: Adil Hasanbasic



INTERNATION UNIVERSITY OF SARAJEVO

ENS203 - ELECTRICAL CIRCUITS I

Lab Report number V - Wheatstone bridge

April 7, 2024

Contents

1	Objective	4
1.1	Wheatstone	4
1.2	Apparatus	4
1.2.1	DC Power Supply	5
1.2.2	Breadboard	5
1.2.3	Resistors	6
1.2.4	Multimeter	7
1.2.5	Potentiometer	7

List of Figures

1	Wheatstone Bridge	4
2	DC power supply	5
3	A breadboard	5
4	Resistors Color Table	6
5	Multimeter	7
6	Potentiometer	7

List of Tables

1	Expected and Measured Resistance Values	6
---	---	---

1 Objective

1.1 Wheatstone

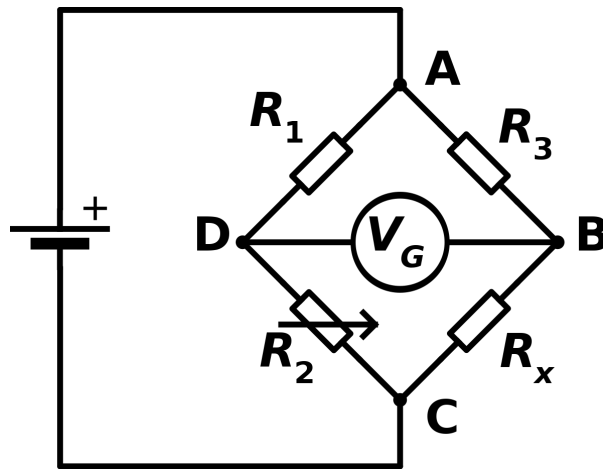


Figure 1: Wheatstone Bridge

The wheatstone bridge is a circuit that is used to measure an unknown resistance. The circuit consists of four resistors, two of which are known, 1 variable resistor, and 1 unknown resistor. The circuit is balanced when the voltage between the two nodes is zero. When the circuit is balanced, the ratio of the two known resistors is equal to the ratio of the two unknown resistors, or in other words

$$\frac{R_1}{R_2} = \frac{R_3}{R_x} \quad (1)$$

then we know that $V_D = V_B$, so the potential difference between the two nodes, V_{DB} , is zero.

In today's lab, we will be using the wheatstone bridge and a multimeter to see when the bridge is balanced.

1.2 Apparatus

- Multimeter
- Potenciometer
- Resistors
- DC Power Supply
- Breadboard

1.2.1 DC Power Supply

Used to provide a constant voltage



Figure 2: DC power supply

1.2.2 Breadboard

A breadboard is a construction base for prototyping of electronics. A breadboard consists of plastic block holding a matrix of electrical sockets of a size suitable for gripping thin connecting wire, component wires or the pins of transistors and integrated circuits (ICs). The sockets are connected inside the board, usually in rows of five sockets.

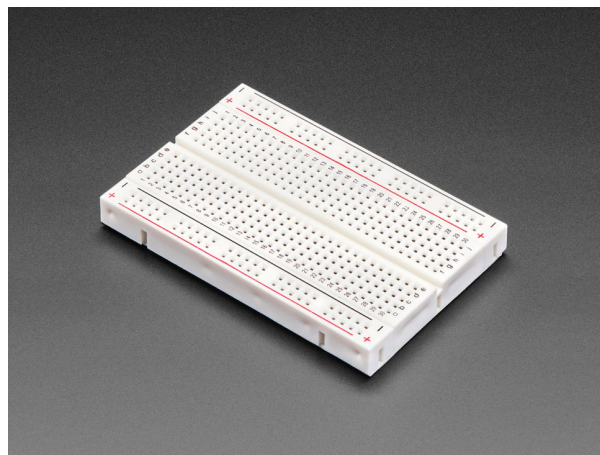


Figure 3: A breadboard

1.2.3 Resistors

As stated before we needed 3 resistors for this lab report so we took 3 resistors with the proper colour code values and then we measured them and marked them.

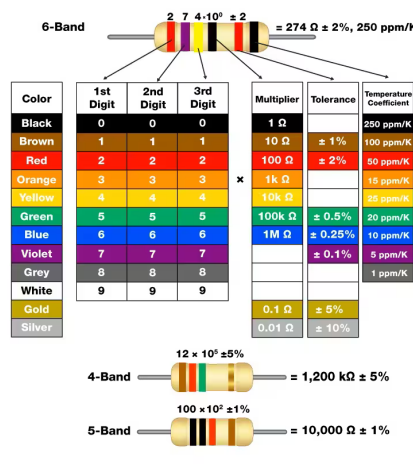


Figure 4: Resistors Color Table

Resistor	Expected Value (Ω)	Measured Value (Ω)
R_1	1000	988
R_3	2200	2142
R_x	2200	2169

Table 1: Expected and Measured Resistance Values

1.2.4 Multimeter

The multimeter is a versatile tool used for measuring various electrical quantities. In this lab, we will use it to measure the voltage drops across components, the currents through branches and components, and the resistance of resistors. To measure voltage drops, connect the multimeter in parallel across the component of interest. Set the multimeter to the voltage measurement mode and select an appropriate range. To measure currents, connect the multimeter in series with the branch or component. Set the multimeter to the current measurement mode and select an appropriate range. To measure resistance, disconnect the resistor from the circuit. Connect the multimeter probes to the resistor terminals. Set the multimeter to the resistance measurement mode and select an appropriate range.



Figure 5: Multimeter

1.2.5 Potentiometer

A potentiometer is a three-terminal resistor with a sliding ,or rotating, contact that forms an adjustable voltage divider as seen in Figure 6. If only two terminals are used, one end and the wiper, it acts as a variable resistor.

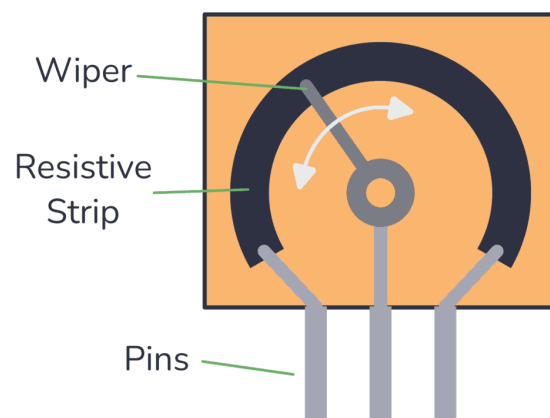


Figure 6: Potentiometer